



Low Dropout Regulator

Electronics project report presented to Eng. Ahmed Amr

Team 8

BN	SEC	ID	Name
35	3	91240727	مروان محمد مبارك سليمان
31	3	91240706	محمود احمد محمود احمد
-	1	9220090	احمد محمد عبدالنبي

1. Introduction

This report presents the design, hand analysis, and simulation verification of a **low-power two-stage OTA** for use in a low-dropout (LDO) regulator. The OTA is implemented in **65 nm CMOS technology** and operates from a **1.2 V supply**, meeting the target specifications for gain, bandwidth, stability, input common-mode range, CMRR, and power consumption.

2. Design Specifications

2.1 Technology Parameters

- Technology: **65 nm CMOS**
- Simulator: **Cadence Spectre**
- Supply Voltage (VDD): **1.2 V**
- Process Corners: **TT, SS, FF**

3. OTA Architecture

3.1 Topology Selection

A two-stage OTA topology was selected for this design. This architecture provides sufficiently high DC gain while remaining compatible with low-voltage operation at a 1.2 V supply. In addition, the two-stage structure allows the use of Miller compensation, which is well suited for stabilizing the amplifier when driving capacitive loads. The chosen topology also enables low power consumption, making it appropriate for LDO applications.

3.2 Circuit Description

The OTA consists of a differential input stage that converts the input voltage difference into a transconductance. An active current mirror load is used in the first stage to increase gain. The output of the first stage drives a second gain stage, which further amplifies the signal and drives the load. To ensure stability in the presence of capacitive loading, a Miller compensation capacitor is connected between the output of the second stage and the intermediate node.

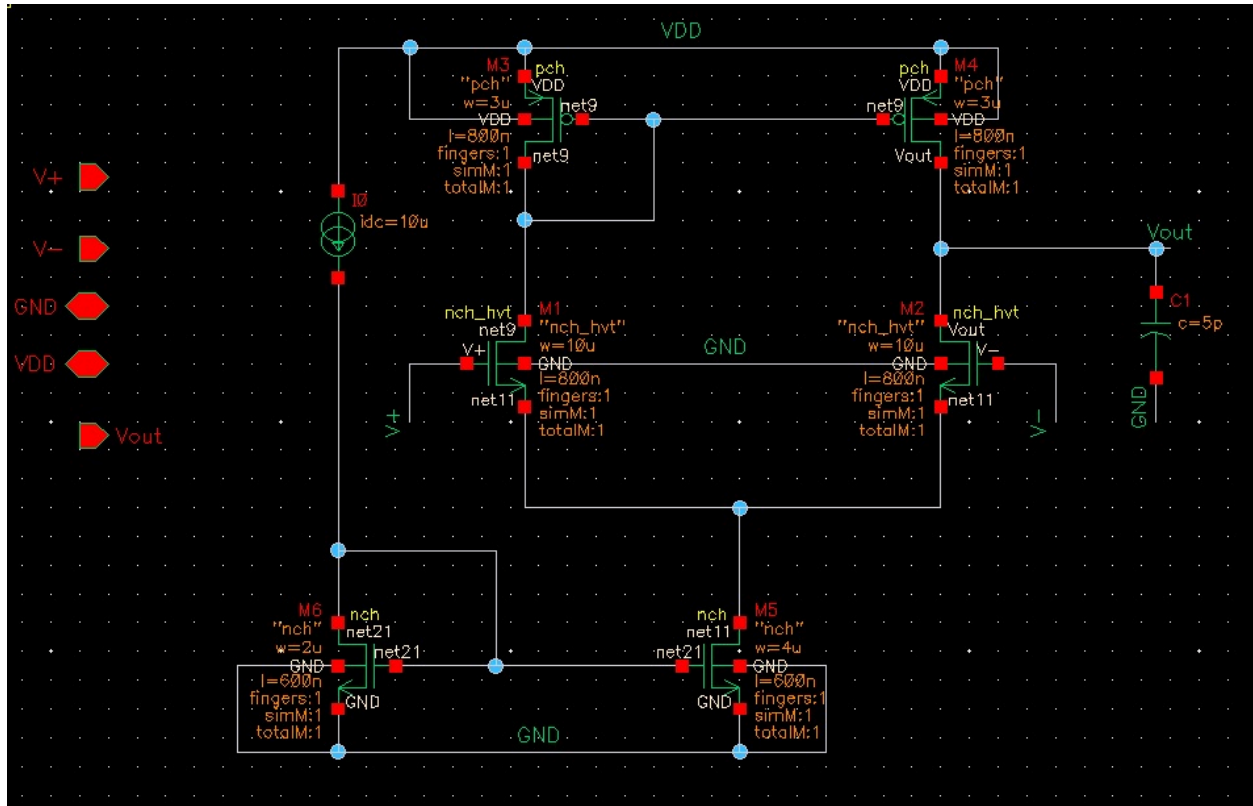


Figure 1: OTA Schematic

4. Design Methodology

4.1 Biasing Strategy

A 10 μA reference current generates all OTA bias currents using current mirrors. The total OTA current is kept below 60 μA. The tail current source is biased at $g_m/I_D = 13$, while the current mirror loads operate within a g_m/I_D range of 8 to 15 to ensure robust operation across process corners.

4.2 Device Sizing Approach

A g_m/I_D -based design methodology is used to systematically meet gain, bandwidth, and power specifications.

Input Differential Pair (M1–M2)

we used nch_hvt (NMOS high V_{th}) to easily achieve the dc gain as it has higher V_{th} with respect to nch (NMOS standard V_{th}).

- $I_{D1,2} = 10\mu A$

- $GBW = \frac{g_{m1,2}}{2\pi C_L}$
- $g_{m1,2} = 2 \cdot \pi \cdot 5p \cdot 5MHz \approx 0.16\mu S$
- $\frac{g_m}{I_D} \approx 16 \text{ S/A}$

To identify **L** we assume **gds** for **NMOS** and **PMOS** are equal

- $A_v = \frac{g_m r_o}{2} = \frac{g_{m1,2}}{2g_{ds1,2}} \geq 50$
- $\frac{g_{m1,2}}{g_{ds1,2}} \geq 100$, $g_{ds1,2} \leq 1.6\mu S$

from **gm/gds** vs **gm/id** chart we got **L = 0.8μ**.

from **ID/W** vs **gm/id** chart we got **W = 10μm**.

Current Mirror Load (M3–M4)

The PMOS loads design by assuming $\frac{g_m}{I_D} = 15 \text{ S/A}$

- $g_{ds3,4} = \frac{I_D}{V_A} \leq 1.6\mu S$, $V_A \geq 6.25$

from **gm/ID** vs **gm/gds Pmos** chart we got **L = 0.8μ**

- $CMIR_{high} = V_{DD} - V_{SG3,4} + V_{thn} \geq 1$
- $V_{sg3,4} \leq 1.2 - 1 + 0.472$, $V_{sg3,4} \leq 0.67$

From **(gm/ID)** vs **VGS** we got **(gm/ID)min = 8 S/A** then from **gm/ID** vs **ID/W**

We got **W = 3μm**

Tail Current Source (M5)

For **ISS = 20μA** and assuming **gm/ID = 13** for moderate inversion.

- $CMRR = \frac{A_v}{A_{vCM}} = 45dB$
- $A_{vCM} \approx \frac{-1}{2g_{m3,4}R_{SS}} = -11dB$
- $g_{ds5} = 45\mu S$, $\frac{g_m}{g_{ds}} \geq 7$

Then **L = 0.6μm**

- $CMIR_{low} = V_{gs1} + V_{dsat5} \leq 0.65 \text{ V}$
- $V_{dsat5} \leq 0.125 \text{ V}$

We got **(gm/ID)min = 11.4**, so we chose **(gm/ID) = 13** to keep some margin.

From **ID/W** design charts we got the required **W = 4μm**.

This ensures sufficient **CMRR ≥ 45 dB** while maintaining the required input common-mode range.

- **Verification**

Final device dimensions are validated through DC operating-point simulations to confirm saturation and compliance with all specifications

Transistor	Input Pair	PMOS load	Tail CS
L(μm)	0.8	0.8	0.6
W(μm)	10	3	4
ID(μA)	10	10	20
gm/ID(S/A)	16	15	13
Vdsat(mV)	77	190	115

5. Simulation Results of the OTA

5.1 DC Operating Point

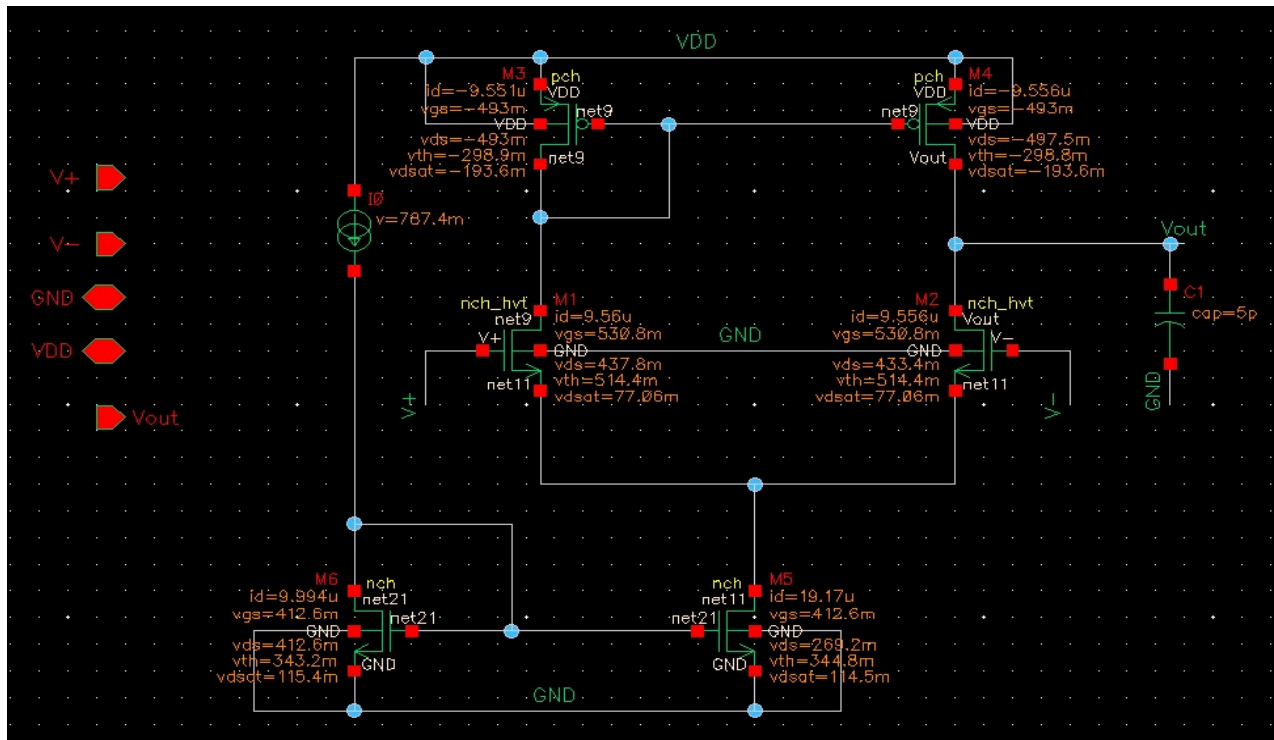


Figure 1: DC Operating Point & MOSFETs' currents

5.2 DC Gain Analysis

DC gain = 38.5 dB

GBW = 5.57 MHz

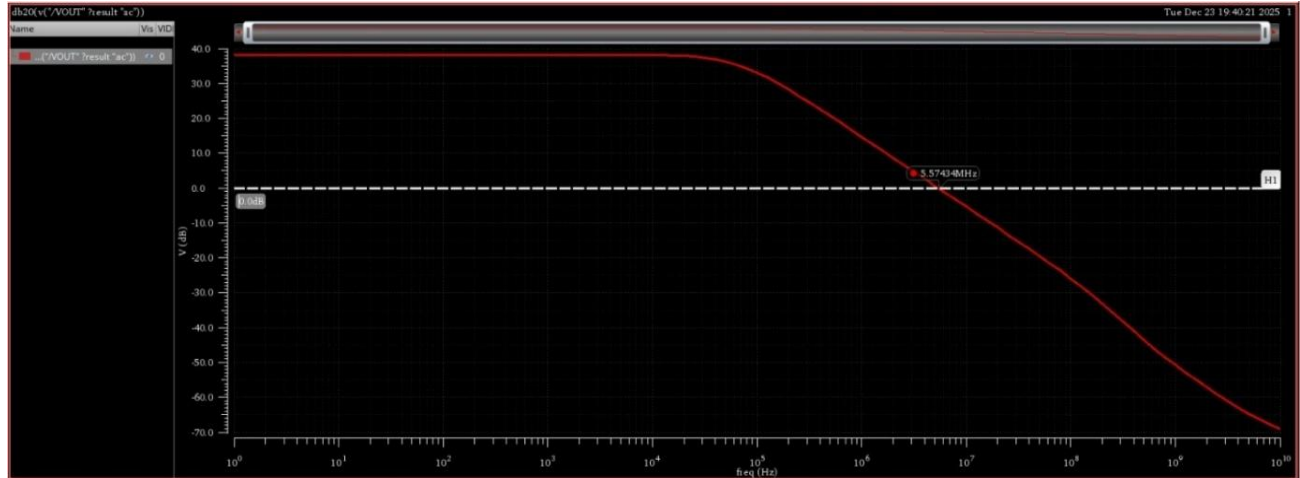


Figure 2: DC gain

5.3 Common-Mode Input Range (CMIR)

$CMIR_{low} = 0.62$

$CMIR_{high} = 1.2$



Figure 3: CMIR

5.4 Stability and Phase Margin

Phase Margin = 89.9 deg

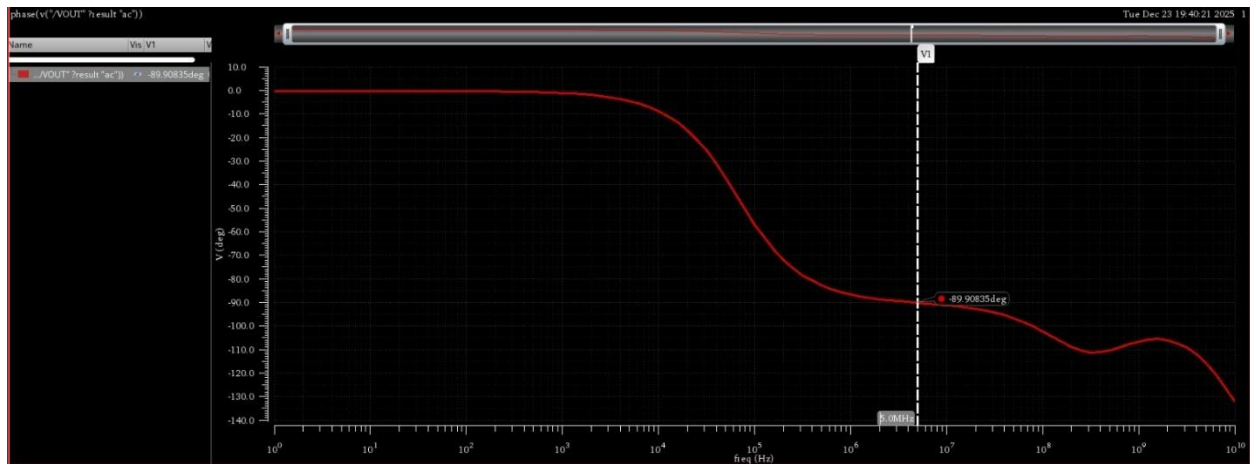


Figure 4: Phase Margin

5.6 Common-Mode Rejection Ratio (CMRR)

CMRR = 70 dB

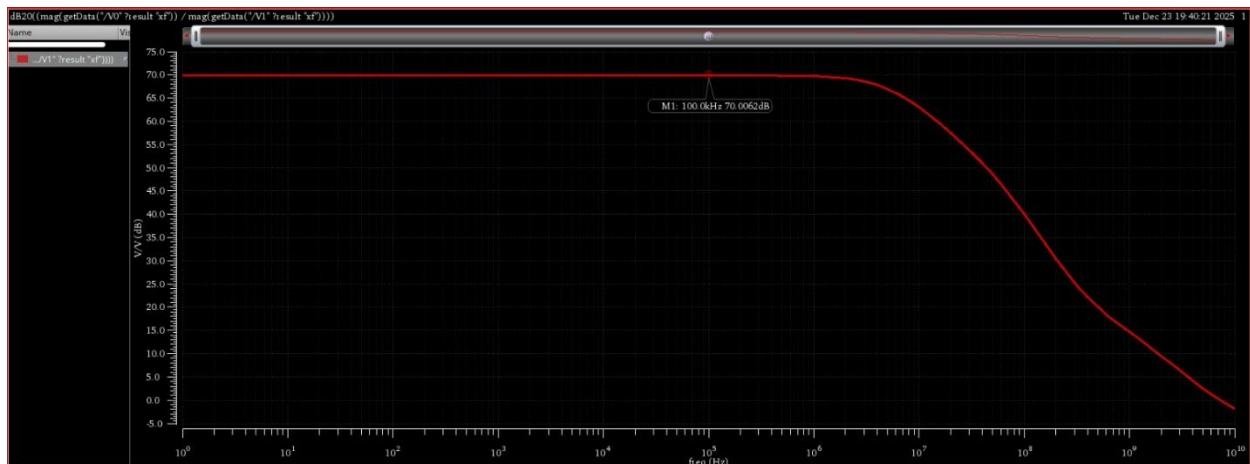


Figure 5: CMRR

5.7 Current Consumption

The OTA Current Consumption is $20\mu A$.

$$V_{OUT}(n) = V_{REF} \left(1 + \frac{R_1 + R_{prog}(n)}{R_2} \right)$$

Programming Step Size

For a desired output voltage step of **50 mV**, the required resistance increment is:

$$\Delta R_1 = \frac{\Delta V_{OUT} \cdot R_2}{V_{REF}} = \frac{0.05 \cdot 30 \text{ k}\Omega}{0.6} \approx 2.5 \text{ k}\Omega$$

R1 Sweep Range

To cover the programmable output range, R_1 is swept from **0 to 15 kΩ**, corresponding to **8 output voltage steps**.

Programmable Output Voltage Table

Step	$R_1(\text{k}\Omega)$	$V_{OUT}(\text{V})$
0	7.50	0.75
1	10.00	0.80
2	12.50	0.85
3	15.00	0.90
4	17.50	0.95
5	20.00	1.00
6	22.50	1.05

6.4 LDO DC Regulation

DC regulation simulations show that the LDO maintains the desired output voltage across the specified range of **0.75 V to 1.05 V**. The output remains stable under nominal load conditions, confirming sufficient loop gain provided by the OTA

6.5 PMOS Pass Transistor Sizing

- PMOS: $W = 10 \mu\text{m}$, $L = 120 \text{ nm}$
- Max load current: $I_D = 30 \mu\text{A}$

On-resistance:

$$R_{\text{ON}} \approx \frac{1}{\mu_p C_{\text{ox}} \frac{W}{L} (V_{\text{SG}} - |V_{\text{TH}}|)}$$

Assuming $\mu_p C_{\text{ox}} \approx 50 \mu\text{A}/\text{V}^2$ and overdrive $V_{\text{SG}} - |V_{\text{TH}}| = 0.2 \text{ V}$:

$$R_{\text{ON}} \approx 1.2 \text{ k}\Omega$$

Dropout voltage:

$$V_{\text{DROP}} = I_{\text{LOAD}} \cdot R_{\text{ON}} = 23.41 \mu\text{A} \cdot 1.2 \text{ k}\Omega \approx 28 \text{ mV}$$



Figure 7: LDO DC Regulation

6.3 Current Consumption

Under nominal operating conditions, the LDO draws $9.994 \mu\text{A}$ from the reference circuit, $18.59 \mu\text{A}$ from the tail current source, and $23.41 \mu\text{A}$ through the pass PMOS. The total current consumption is therefore:

$$I_{TOTAL} = 9.994 + 16.78 + 20.08 = 46.83 \mu A$$

This total current is **below 60 μA** , confirming low-power operation while maintaining stable regulation.

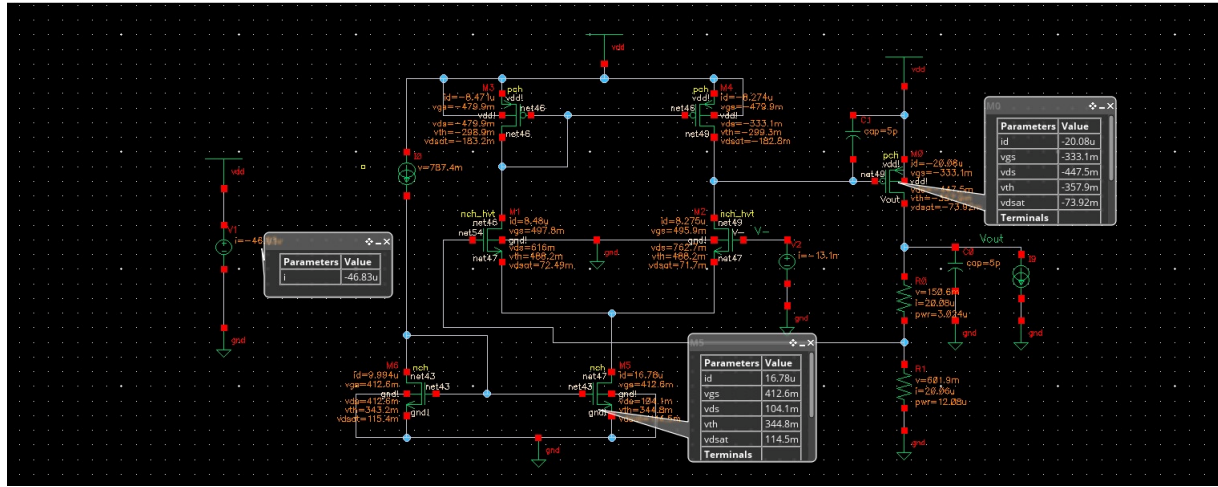


Figure 8: LDO Current Consumption

7. LDO PSRR (Power Supply Rejection Ratio)

PSRR = -58.6dB

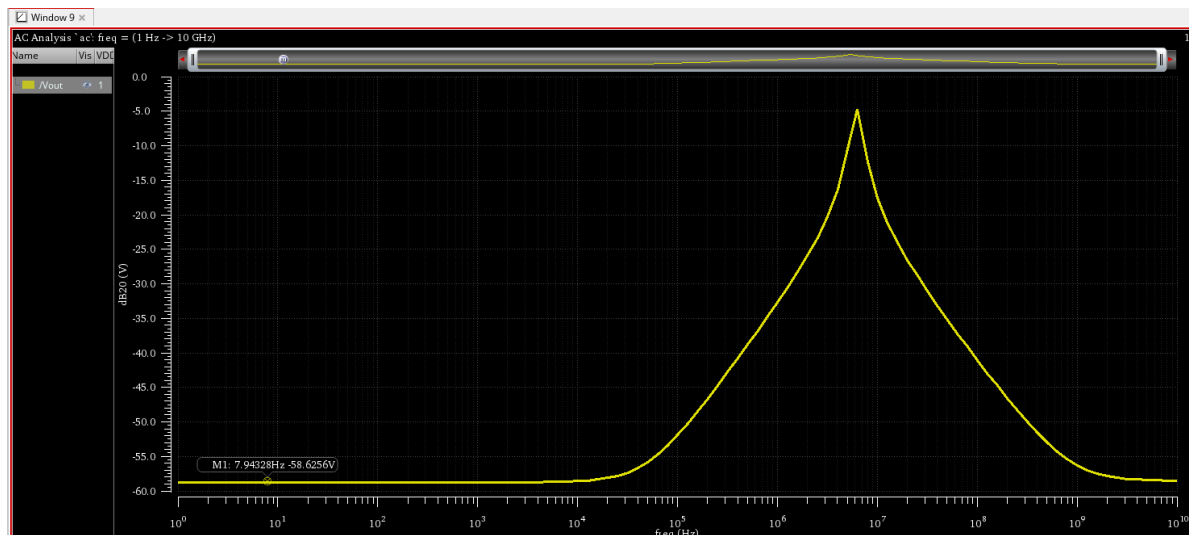


Figure 9: LDO PSRR

8. LDO PVT Analysis

PVT Analysis and Output Voltage Accuracy

A PVT analysis was performed to verify LDO robustness. The **nominal output voltage** at the typical corner is for each range is

752.57mV , 802.65mV , 852.92mV , 903.01mV , 953.03mV , 1.003V , 1.053V

Across all PVT the worst-case deviation is $\pm 1.5 \text{ mV}$ ($\pm 0.2\%$), confirming stable regulation across PVT variations.

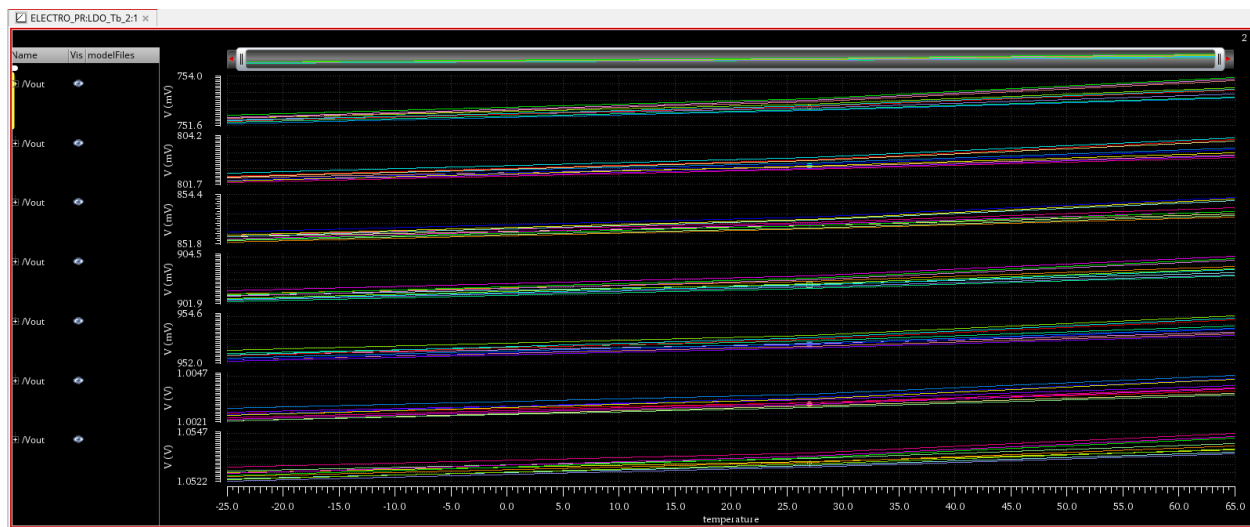


Figure 10: LDO PVT